


More Series LED Circuits

by erkrystof - Thursday, August 05, 2010

<http://www.hoverandsmile.com/more-series-led-circuits/>

So, last time we introduced the simple LED circuit. A power supply (your battery), an LED (the light), and a resistor (to limit current). We introduced all the math you'd need to calculate this, but hey, let's not stand in the way of progress! Check out these links for online LED calculators that give you the exact resistance you'll need to handle whatever LED wiring configurations you like:

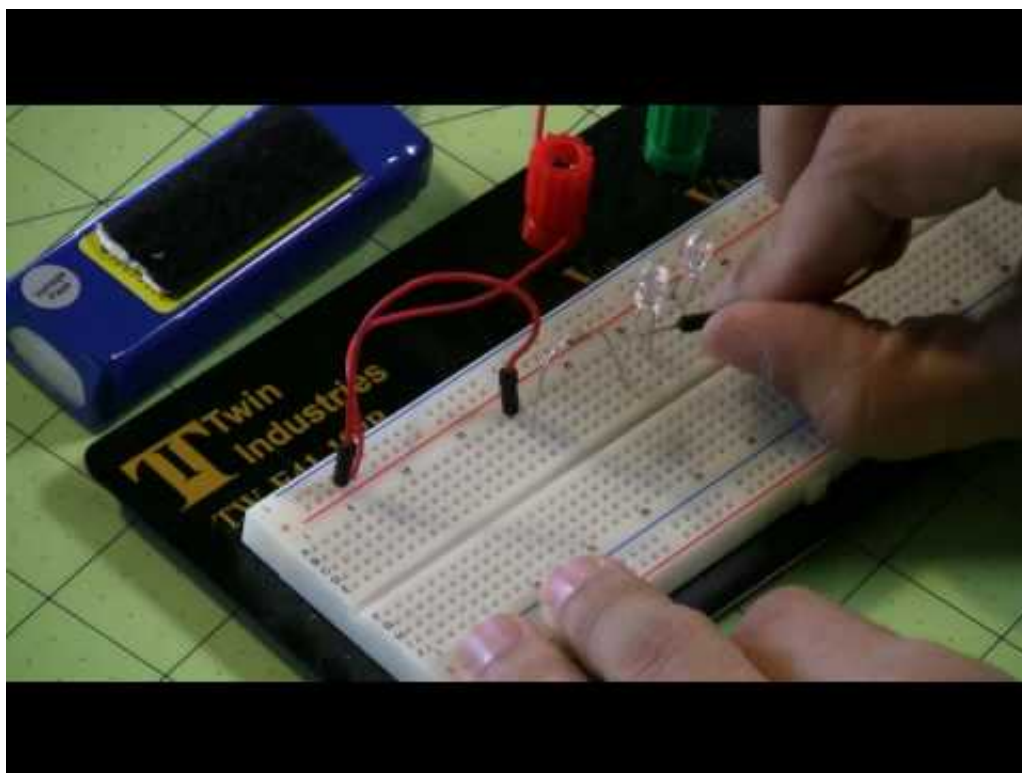- [LED Wizard](#)
- [LED Calculator](#)
- [HB LED Calc](#)



The example below is from the LED Wizard.

12.6	Source voltage
3.3	diode forward voltage
20	diode forward current (mA)
1	number of LEDs in your array
View output as: <input type="radio"/> ASCII <input type="radio"/> schematic <input checked="" type="radio"/> wiring diagram	
<input checked="" type="checkbox"/> help with resistor color codes	
<input type="button" value="design my array"/>	

The wizard thinks arrays of a single LED are cool too.

Solution 0: 1 x 1 array uses 1 LEDs exactly



The wizard says: In solution 0:


- each 470 ohm resistor dissipates 188 mW
- the wizard says the color code for 470 is yellow violet brown
- the wizard thinks 1/2W resistors are needed for your application
- together, all resistors dissipate 188 mW
- together, the diodes dissipate 66 mW
- total power dissipated by the array is 254 mW
- the array draws current of 20 mA from the source

www.hoverandsmile.com, source from LED wizard at <http://led.linear1.org/led.wiz>

LED Wizard Sample Output

It tells us, just like our calculations did, that we need a 470 Ohm resistor. It's much faster than doing the calculations yourself, but at least this way you *know* what calculations it's doing for you.

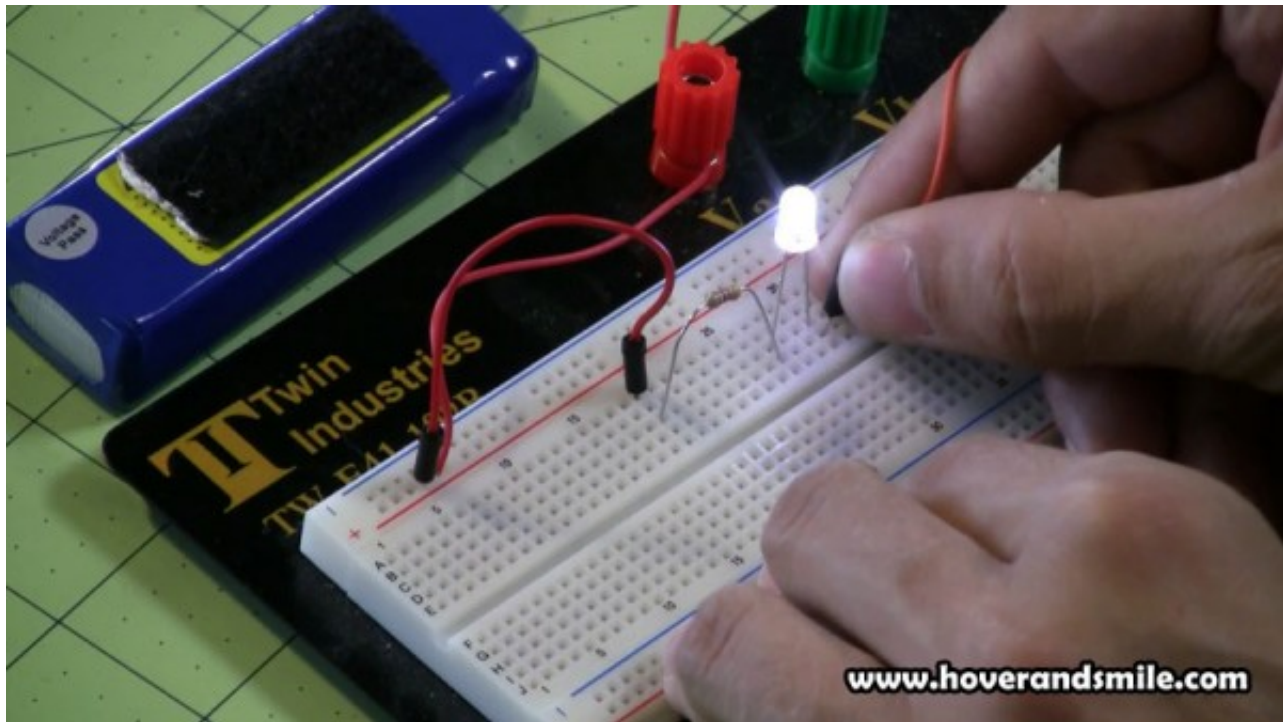And here is a single LED with a 470 Ohm Resistor. A perfect match, lighting up nicely.



Simple single resistor LED Circuit

Now, since that lights up ONE LED, what happens if I plug another 3.3 Volt LED in series? I'm limiting my current already with the resistor, so it won't burn out, but will happen is that both LEDs will light up, but not as bright as one alone. This is because we've changed that sum of forward voltage. Time to re-calculate!

Resistance = $(12.6 - 2 * 3.3) / .02 = 300 \text{ Ohms}$ (although some wizards will say 330 as it's a more common resistance value)

So now, if I use just two LEDs, I need to lower my resistance. If I use three LEDs, I lower it some more!

Why? Well, say we used 470 ohms with 2 LEDs. *Our current drops!* With a little algebra the equation would look like this using the first 470 Ohm resistor:


$$470 = (12.6 - 2 * 3.3) / I$$

$$I = (12.6 - 2 * 3.3) / 470$$

$$I = .012 \text{ amps} = 12 \text{ milliamps}$$


Only 12 milliamps is allowed through the circuit now. That's not as bright! We must lower the resistance of the circuit to allow the two LEDs to light up just as bright as the single LED because we've changed the voltage drops (even if the supply 12.6 volts remains the same). It's all proportional. More voltage drops requires less resistance to maintain the proper current. Add an LED, remove an LED, and you must recalculate!

With an example forward voltage of 3 volts per LED and power supply of 9 Volts, you could wire up all 3 LEDs in series and not need a resistor at all (although a resistor is still a good idea with LEDs – even a single Ohm resistor). However, say you wanted to wire four LEDs? If you wired them in series, you'd get 'no-joy'. The sum of forward voltage of your LEDs has to be less than your supply voltage.

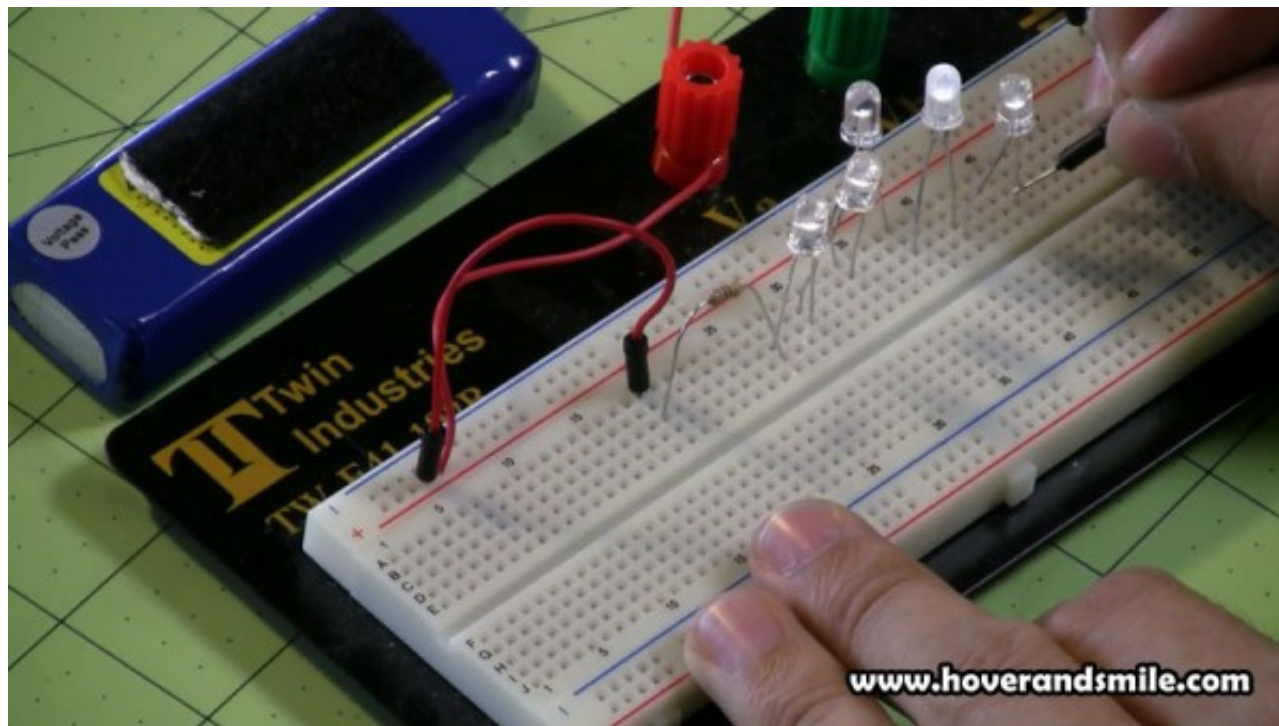

LEDs in series

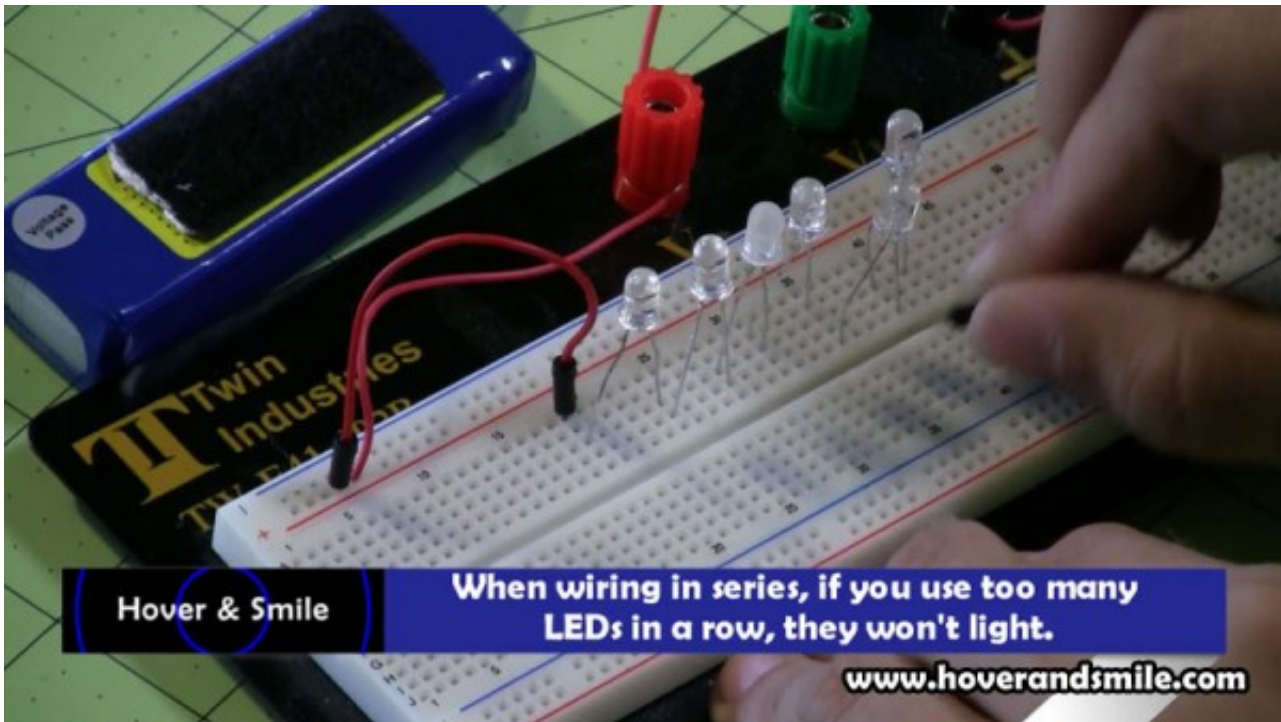Here we have the same 470 Ohm resistor but with 5-6 LEDs. Each time we add an LED in series we get less light, and if the sum of our forward voltage (add up all the LED forward voltage numbers) is greater than our power supply of 12.6, you'll either get dimly lit lights, or NO lighting at all.



Too many LEDs for 12.6 volts wired in series, resistor or not.



Series LED Diagram

Vinnie says that if you use too many LEDs in series, they won't light up, depending on how many volts of supply you use.

If you can only light so many in series, how do you add more LEDs?

PARALLEL CIRCUITS

If you've looked at the LED calculators or watched this movie by now, you may have noticed that if I have 1 LED, 2 LEDs, or 3 LEDs in series, although the voltage drops increase, my current does not. I'm still only pulling .02 amps through the circuit.

But if we have to wire LEDs in parallel to get more to light up than just a couple, *each parallel line* will have it's own separate current draw. So with parallel circuits, your current will increase.

We'll go over the parallel circuits in the next part!

Comments? (0)

Tags for this article: [electronic-circuits](#), [LED](#), [night flying](#)

PDF source - www.hoverandsmile.com