


## Wiring Standard Bulb LEDs

by erkrystof - Saturday, August 07, 2010

<http://www.hoverandsmile.com/wiring-standard-bulb-leds/>

We'll use 3 White LEDs from Radio Shack, wired in series. Two pairs of this circuit will be created, one for each side of the craft. One of the LEDs points to the rudder, and the other two will be placed at opposite ends of a straw to make a 'tube of light' on the top side of our Combat! flyer.


### Your standard Bulb LED

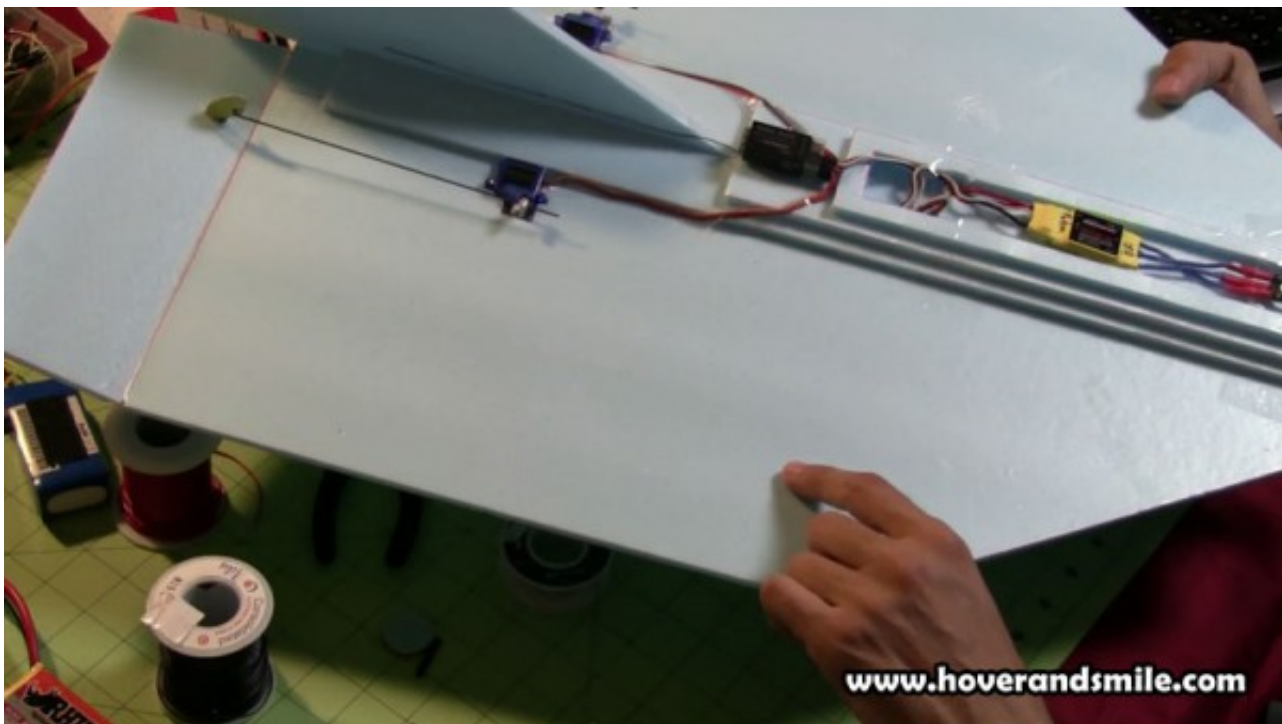
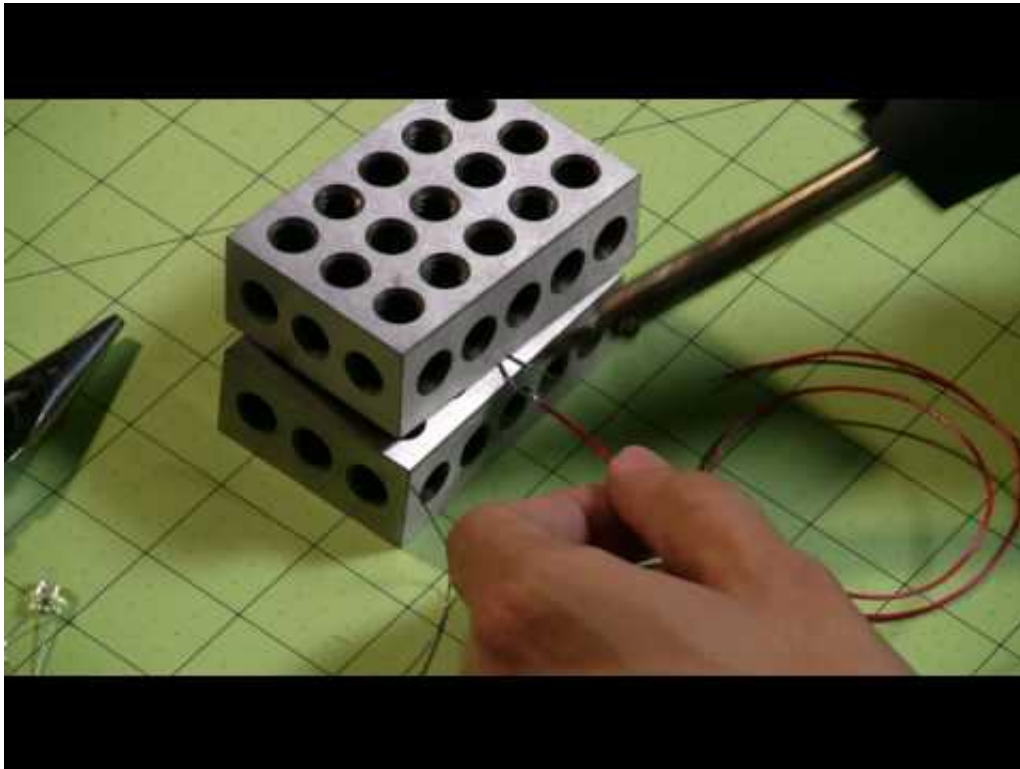
#### LED Placement Testing

To calculate the resistor values you'll need, you can reference our earlier articles on how to do that manually, or just use one of these handy little web resistance calculators:

- [LED Wizard](#)
- [LED Calculator](#)
- [HB LED Calc](#)




Since in our example we have 12.6 volts from our 3S battery (that's the maximum of course – the battery

will have less voltage over time as we discharge it). Our Radio Shack LED package says that the lights have a mcd rating of 7000 (bright!), have a forward voltage of 3.6 volts, and require a current of 20 milliamps (.02 amps).

So, plugging that into our calculator, we get 100 ohms as our resistance value required to wire up all three LEDs in series for our example power supply.

12.6	Source voltage <a href="#">?</a>
3.6	diode forward voltage <a href="#">?</a>
20	diode forward current (mA) <a href="#">?</a>
3	number of LEDs in your array
View output as: <input type="radio"/> ASCII <input type="radio"/> schematic <input type="radio"/> wiring diagram <a href="#">?</a>	
<input type="checkbox"/> help with resistor color codes	
<input type="button" value="design my array"/>	

Solution 0: 3 x 1 array uses 3 LEDs exactly




The wizard says: In solution 0:

- each 100 ohm resistor dissipates 40 mW
- the wizard thinks 1/4W resistors are fine for your application [?](#)
- together, all resistors dissipate 40 mW
- together, the diodes dissipate 216 mW
- total power dissipated by the array is 256 mW
- the array draws current of 20 mA from the source.
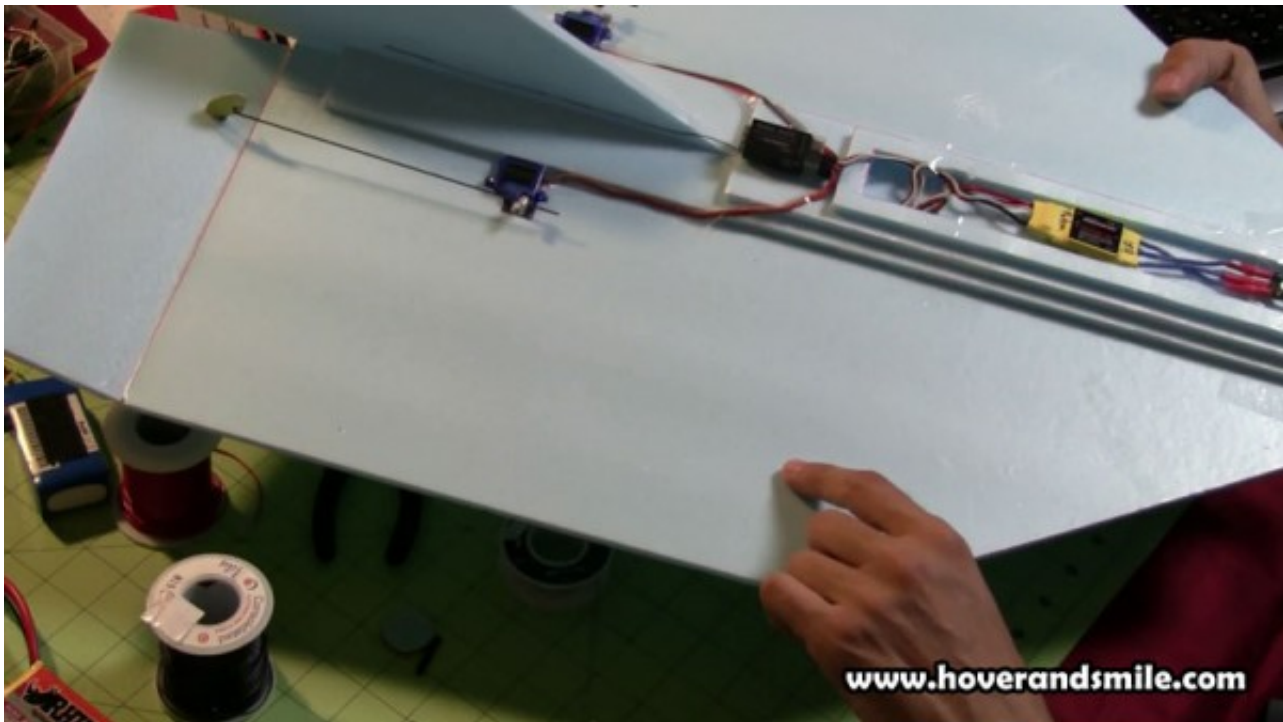
## Bulb LED Diagram

I don't have a 100 Ohm resistor, but I can use the next highest number that I *do* have, which is 110 Ohms.

Now that we have the parts we need, take one last look at our naked top side of our flyer as we mentally measure out the wire lengths for our craft.




## LED Placement Testing

We'll use one length of red wire to help us remember the positive end, and the rest will be black.


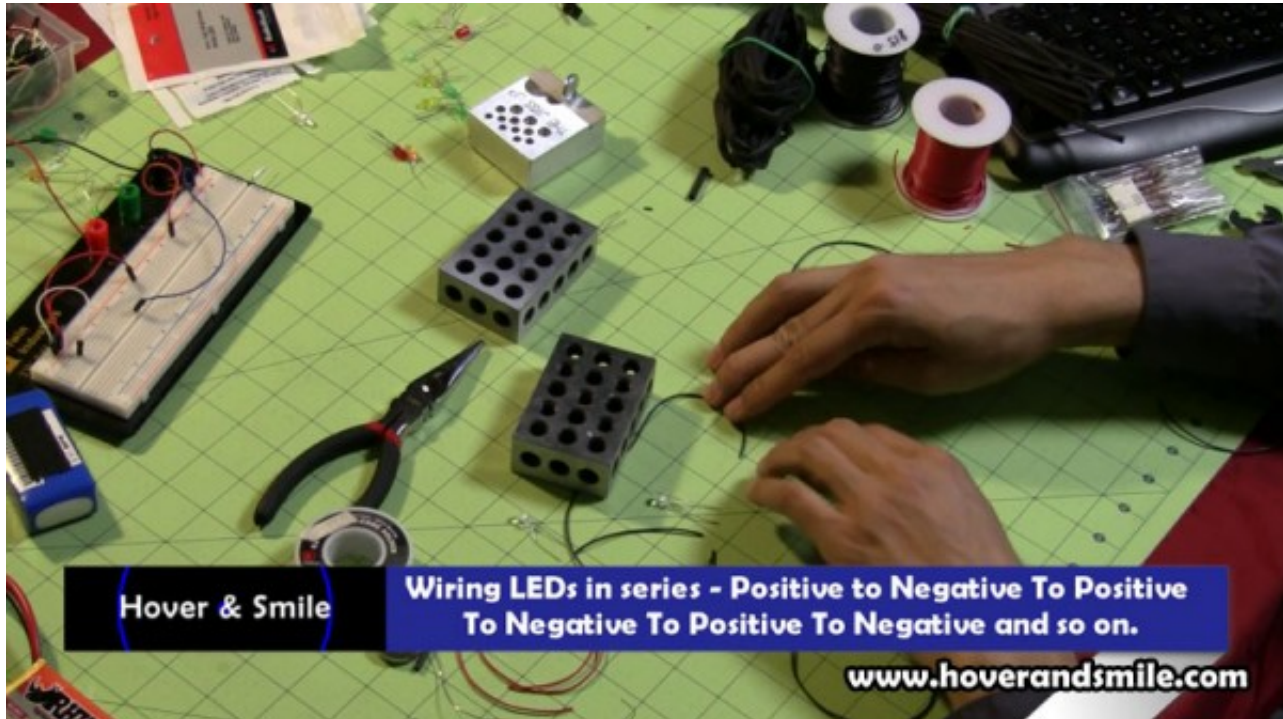
## Cutting out our wires

As for the wiring order, look at the wiring diagram from the LED wizard. You can see that the LEDs are wired from positive to negative all the way down the line. So the negative lead from the first LED will connect to the positive lead of the second LED, and so on.



## Cutting out our wires

As we strip insulation from the wire ends, we'll need to 'tin' our wires and LEDs with some solder by quickly and simply heating the wire with the soldering iron and letting solder flow onto the wire tip.



Soldering the LED to the wire is simply a matter of connecting the two pieces and heating the tinned elements with the soldering iron.



At the end of the wiring line, just before the last wire, we'll go ahead and solder our tinned resistor:



Now, a great way to protect your circuit is to have some shrink tube, or electrical tape, anything to wrap around the wires and keep them from short circuiting, as well as protecting the elements. I prefer the shrink tube method here, so we've cut small pieces and slid them over the wires as we wired up our circuit.

Then, with a simple flame or heat gun, heat the shrink tube to condense it over our circuit. Just be careful with the flame, don't burn the electronics, wires, or yourself!



Finally, our circuit is complete, and we can test it by taking the positive and negative ends and attaching

them to our battery. In the next article, we'll go over a little bit more difficult LED handling – SMD LEDs, the tiny strip LEDs you can also buy individually and wire your own circuits up with. Fun, but *tiny*!



Testing the circuit

## Comments? (0)

Tags for this article: [electronic-circuits](#), [LED](#), [night flying](#)

---

PDF source - [www.hoverandsmile.com](http://www.hoverandsmile.com)